



Chapter 2

二極體電路


2.1 整流電路

南方科技大學

Southern Taiwan University

2.1 整流電路


1. 半波整流

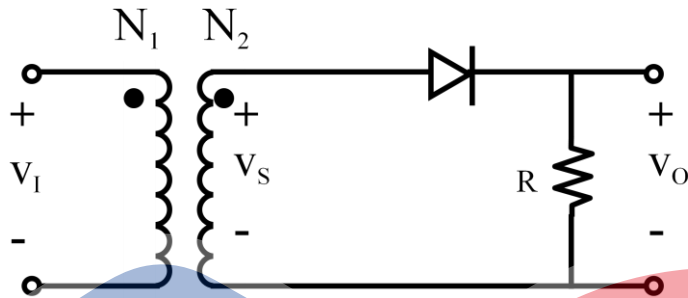


$$V_1 = V_1(\text{rms}) \cdot \sqrt{2}$$

$$V_s = V_s(\text{rms}) \cdot \sqrt{2}$$
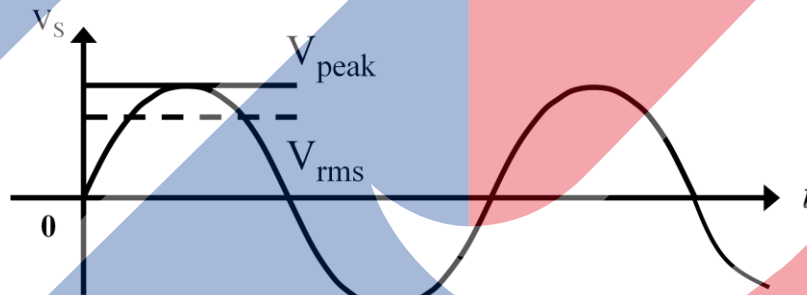
$$\frac{V_1}{V_s} = \frac{N_1}{N_2} \text{ (變壓器圈數比)}$$


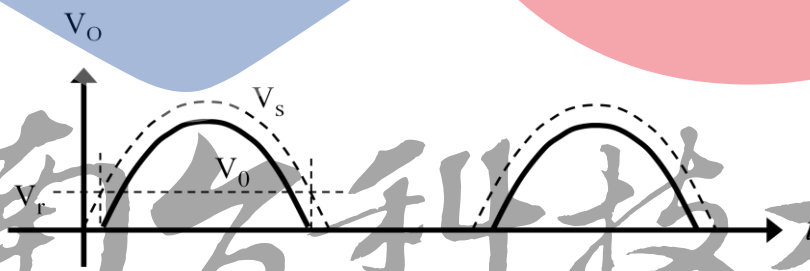
$$V_{\text{rms}} = \frac{V_{\text{peak}}}{\sqrt{2}}$$




$$i_D = \frac{V_s - V_Y}{R_L}$$

When $V_s > V_Y$, $V_0 = V_s - V_Y$

When $V_s < V_Y$, $V_0 = 0$

2. 全波整流


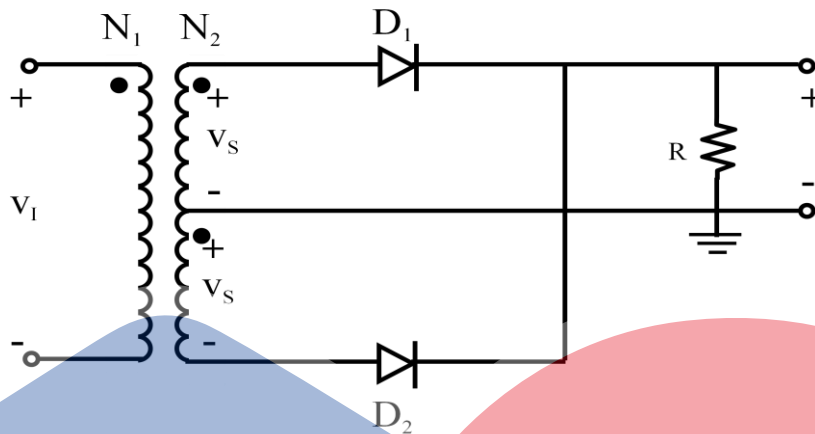


When $V_S > V_Y$, $V_{out} = V_S - V_Y$ (D_1 ON D_2 OFF)

$$V_{o(peak)} = V_M - V_Y$$

When $V_S < -V_Y$, $V_{out} = -V_S + V_Y$ (D_1 OFF D_2 ON)
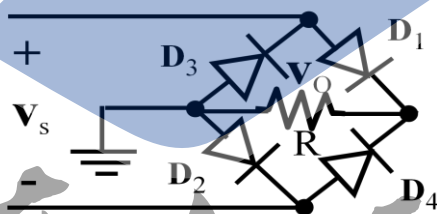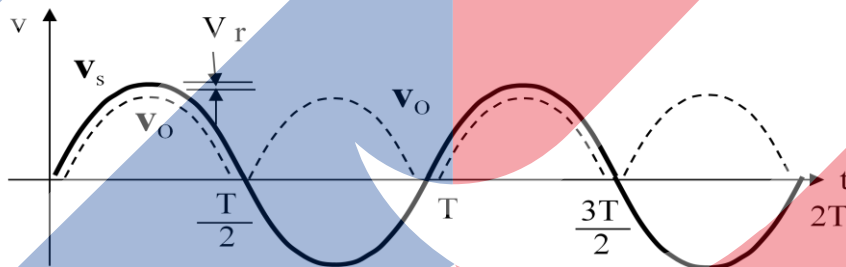
$$V_{o(peak)} = -(-V_M) - V_Y = V_M - V_Y$$




When $V_1 > 2V_Y$, $D_1 D_2$ ON, $D_3 D_4$ OFF


$$V_o = V_s - 2V_Y$$

When $V_1 < -2V_Y$, $D_3 D_4$ ON, $D_1 D_2$ OFF

$$V_o = V_s - 2V_Y$$

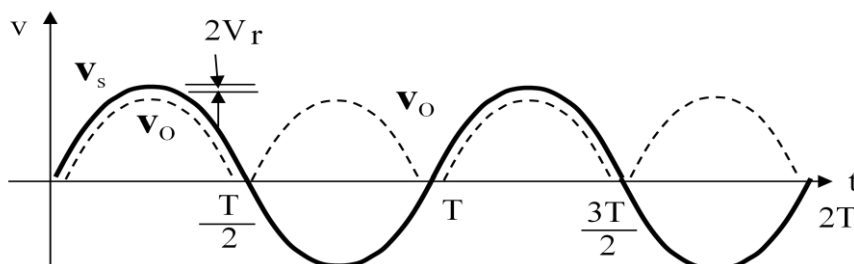


Southern Taiwan University

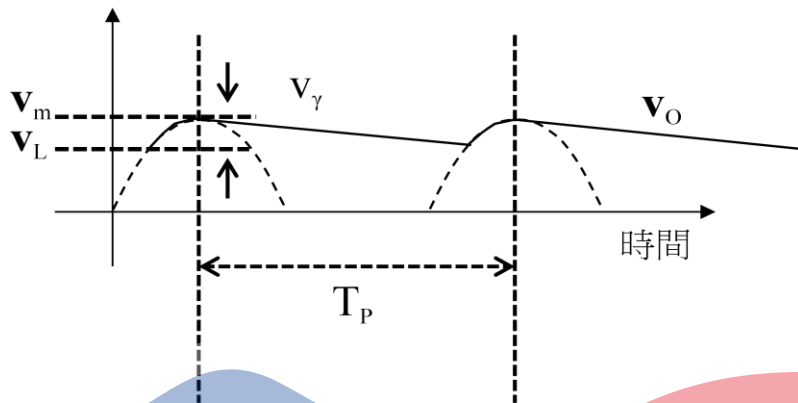

$$V_L = V_m e^{-\frac{T}{RC}}, \text{ T 為 RC 放電時間}$$

漣波電壓(Ripple Voltage)
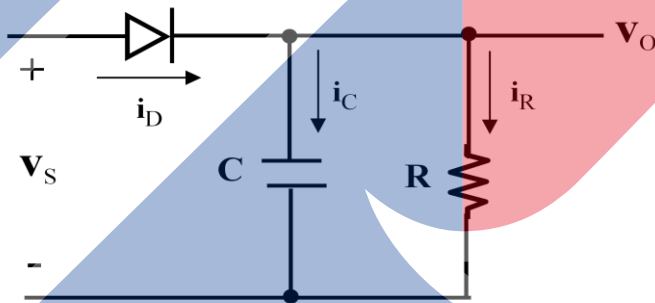
$$V_{\text{ripple}} = V_m - V_L = V_m - V_m e^{-\frac{T}{RC}} = V_m (1 - e^{-\frac{T}{RC}})$$



假設 $T \ll RC$


$$e^{-\frac{T}{RC}} \cong 1 - \frac{T}{RC} \text{ 代入上式}$$

$$V_{\text{ripple}} = V_m \left(1 - \left(1 - \frac{T}{RC} \right) \right) \cong V_m \left(\frac{T}{RC} \right) \cong V_m \left(\frac{T_P}{RC} \right) = V_m \frac{1}{RCf} \text{ (半波)}$$

$$V_{\text{ripple}} = V_m \left(\frac{T_P}{2RC} \right) = V_m \frac{1}{2RCf} \text{ (全波)}$$

南方科技大學

Southern Taiwan University

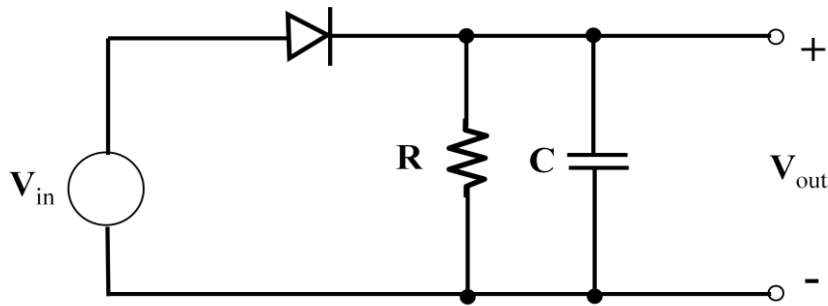

充電:

$$i_D = i_C + i_R = C \frac{dV_O}{dt} + \frac{V_O}{R} \{t = 0^- \text{附近} \cdot V_O \cong V_m \cos\omega(-\Delta t) = V_m \cos\omega(\Delta t)\}$$

$$\because \Delta t \rightarrow 0$$

$$\Rightarrow \omega\Delta t \rightarrow 0 = 1 - \frac{1}{2}(\omega\Delta t)^2$$

$$V_O = V_m \cos\omega(\Delta t) = V_m \left[1 - \frac{1}{2}(\omega\Delta t)^2 \right] = V_m - V_{\text{ripple}}$$

$$V_m - V_m \left[\frac{1}{2}(\omega\Delta t)^2 \right]$$

$$V_{\text{ripple}} = V_m \left[\frac{1}{2}(\omega\Delta t)^2 \right]$$

$$(\omega\Delta t)^2 = \frac{2V_{\text{ripple}}}{V_m}$$

$$\omega\Delta t = \sqrt{\frac{2V_{\text{ripple}}}{V_m}}$$

求 $i_{D(\max)}$

$$i_{D(\max)} = i_{C(\max)} + \frac{V_m}{R}$$

$$i_{C(\max)} = C \frac{dV_O}{dt} (t = -\Delta t)$$

$$= C \frac{dV_m \cos\omega(t)}{dt} (t = -\Delta t)$$

$$= -CV_m \omega \sin\omega(\Delta t)$$

$$= CV_m \omega (\omega\Delta t)$$


$$= CV_m \omega \sqrt{\frac{2V_{\text{ripple}}}{V_m}}$$

南方科技大學
Southern Taiwan University

$$= CV_m \frac{V_m \pi}{V_{\text{ripple}} RC} \sqrt{\frac{2V_{\text{ripple}}}{V_m}} = 2\pi \frac{V_m}{R} \sqrt{\frac{V_m}{2V_{\text{ripple}}}}$$

$$\begin{aligned} i_{D(\text{avg})} &= i_{C(\text{avg})} + \frac{V_m}{R} \\ &= \frac{CV_{\text{ripple}}}{\Delta t} + \frac{V_m}{R} \\ &= \frac{CV_{\text{ripple}}}{\frac{RCV_{\text{ripple}}}{\pi V_m}} \sqrt{\frac{V_m}{2V_{\text{ripple}}}} + \frac{V_m}{R} \\ &= \frac{\pi}{R} V_m \sqrt{\frac{V_m}{2V_{\text{ripple}}}} + \frac{V_m}{R} \\ &= \frac{V_m}{R} \left(1 + \pi \sqrt{\frac{V_m}{2V_{\text{ripple}}}} \right) \Rightarrow 2i_{D(\text{avg})} = i_{D(\text{max})} \end{aligned}$$

◆ 倍壓電路(Voltage Doubler Circuit)

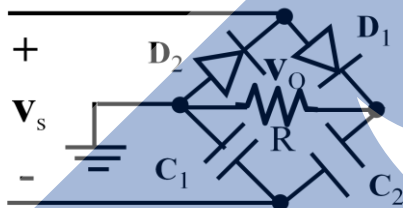

When $V_s < V_Y$ 時

$D_1 \rightarrow \text{OFF}$

$D_2 \rightarrow \text{ON}$

電容 C_1 充電至 $V_s - V_Y$

峰值此時 $V_{C1,2} = V_Y - V_o$

When $V_s > V_Y$ 時

$D_1 \rightarrow \text{ON}$

$D_2 \rightarrow \text{OFF}$

因此時電容 C_1 電壓為 $V_{C1,2} = V_s - V_Y$

同時對 C_2 充電

則 $V_o = V_s - V_Y + V_s - V_Y = 2V_s - 2V_Y \cong 2V_m$

第三半周時 電容不在充電