

## Chapter 2


### 二極體電路

2.3 剪波器(Clippers)與夾波器(Clampers)電路



南方科技大学  
Southern Taiwan University

## 2.3 剪波器(Clippers)與夾波器(Clampers)電路

### ◆ 單一二極體的剪波電路(Clippers)

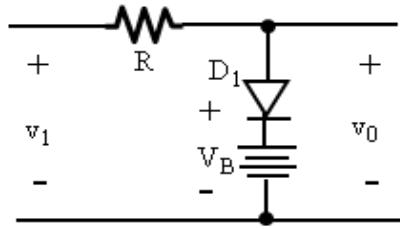

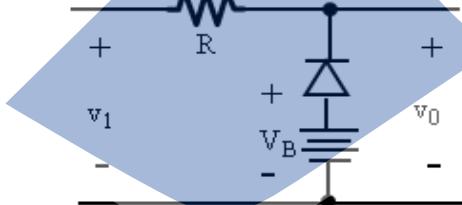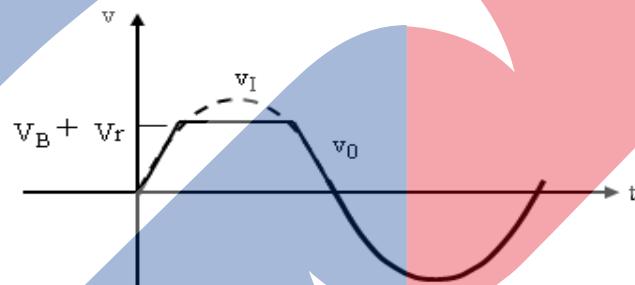
When  $V_i > V_B + V_\gamma$   
 $D \rightarrow \text{ON} \quad V_o = V_B + V_\gamma$   
 When  $V_i < V_B + V_\gamma$   
 $D \rightarrow \text{OFF} \quad V_o = V_i$




When  $V_D > V_\gamma$   
 $D \rightarrow \text{ON} \quad V_o = V_B - V_\gamma$   
 When  $V_B - V_\gamma \leq V_i$   
 $D \rightarrow \text{OFF} \quad V_o = V_i$



Southern Taiwan University

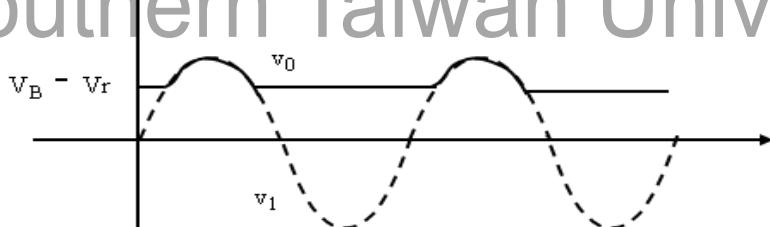

◆ 兩個二極體的剪波電路(Clippers)

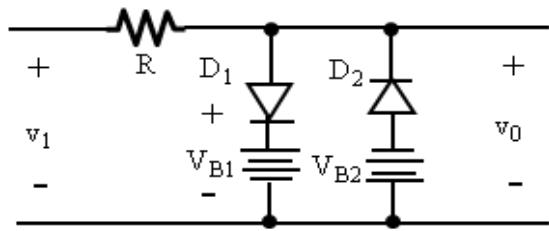

A.  $D_1 \rightarrow \text{OFF}$   $D_2 \rightarrow \text{OFF}$

$$V_o = V_i$$

B.  $D_1 \rightarrow \text{ON}$   $D_2 \rightarrow \text{ON}$

$$V_o = V_{B1} + V_{\gamma 1}$$

$$V_o = -(V_{B2} + V_{\gamma 2})$$


此情況不可能發生

C.  $D_1 \rightarrow \text{ON}$   $D_2 \rightarrow \text{OFF}$

$$V_o = V_{B1} + V_{\gamma 1}$$


D.  $D_1 \rightarrow \text{OFF}$   $D_2 \rightarrow \text{ON}$

$$V_o = -(V_{B2} + V_{\gamma 2})$$

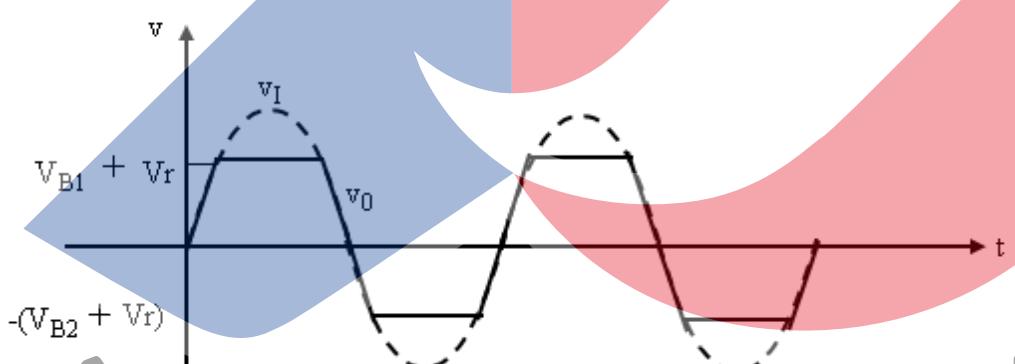

南方科技大学  
Southern Taiwan University

◆ 單一二極體的夾波器(Clampers)

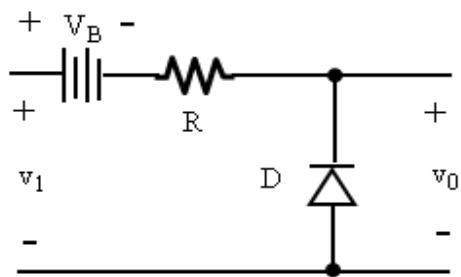

When D ON

$$V_O = -V_\gamma$$

$$V_D = V_B - V_i > V_\gamma$$


$$\boxed{V_B - V_\gamma > V_i}$$

When D OFF

$$V_O = V_\gamma - V_B$$

$$V_D = V_B - V_i \leq V_\gamma$$

$$\boxed{V_B - V_\gamma \leq V_i}$$

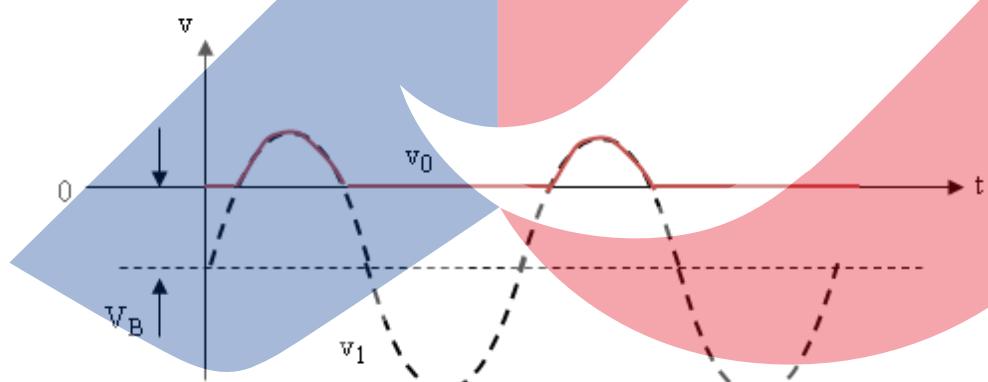

南台灣科技大學  
Southern Taiwan University