



Chapter 4. 基本場效電晶體 (FET)放大器(Basic FET Amplifiers)

4.6 單級積體 MOSFET 放大器

南方科技大学
Southern Taiwan University

4.6 單級積體 MOSFET 放大器

1. 具增強型負載的 NMOS 放大器

AC 分析

A. 畫出等效電路圖

B. 參數計算

$$g_{mL} = 2\sqrt{k_n L I_{DQ}} \quad r_{oL} = (\lambda I_{DQ})^{-1}$$

$$g_{mD} = 2\sqrt{k_n D I_{DQ}} \quad r_{oD} = (\lambda I_{DQ})^{-1}$$

C. 求 A_V 、 R_{in} 、 R_{out}

$$V_{gsL} = -V_O \quad V_{gsD} = V_i$$

$$i_{roD} = \frac{V_O}{r_{oD}} \quad i_{roL} = \frac{V_O}{r_{oL}}$$

$$\text{A點 KCL: } g_{mD}V_{gsD} + i_{roD} + i_{roL} - g_{mL}V_{gsL} = 0$$

$$\rightarrow g_{mD}V_i + \frac{V_O}{r_{oD}} + g_{mL}V_O + \frac{V_O}{r_{oL}} = 0$$

$$\rightarrow V_O \left(\frac{1}{r_{oD}} + g_{mL} + \frac{1}{r_{oL}} \right) = -g_{mD}V_i$$




$$A_V = \frac{V_O}{V_i} = \frac{-g_{mD}}{\left(\frac{1}{r_{oD}} + g_{mL} + \frac{1}{r_{oL}} \right)} = \frac{-g_{mD}}{\left(\frac{1}{r_{oD}} + \frac{1}{g_{mL}} + \frac{1}{r_{oL}} \right)} = -g_{mD}(r_{oD} \parallel \frac{1}{g_{mL}} \parallel r_{oL})$$

$$\text{When: } \frac{1}{g_{mL}} \ll r_{oD}, r_{oL}$$

$$A_V \approx -\frac{g_{mD}}{g_{mL}} = \frac{-2\sqrt{k_n D I_{DQ}}}{2\sqrt{k_n L I_{DQ}}} = -\sqrt{\frac{k_n D}{k_n L}} = -\sqrt{\frac{(\frac{W}{L})_D}{(\frac{W}{L})_L}}$$

$$R_{in} = r_{oD} \parallel r_{oL}$$

$$R_{out} = \infty$$

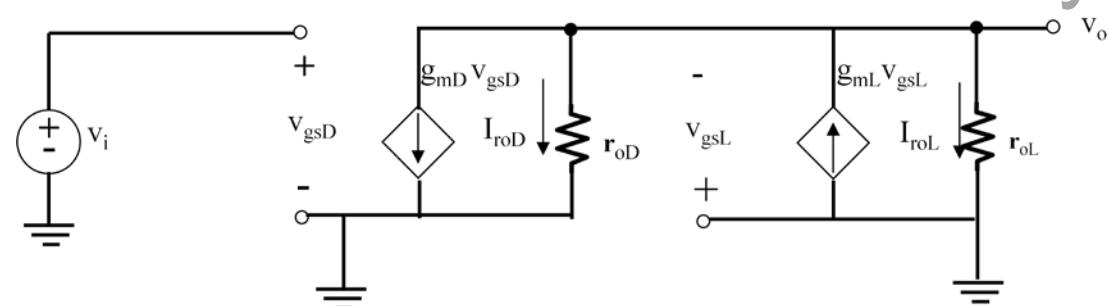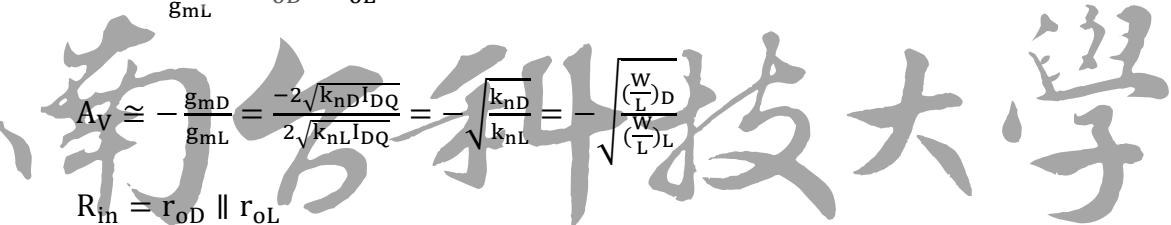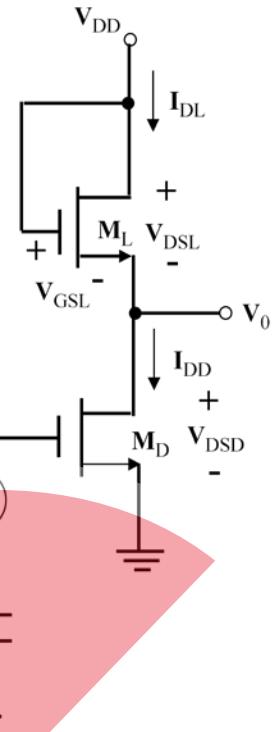

2. 具空乏型負載的 NMOS 放大器

AC 分析

A. 畫出等效電路圖

B. 參數計算

$$g_{mL} = 2\sqrt{k_n L I_{DQ}} \quad r_{oL} = (\lambda I_{DQ})^{-1}$$

$$g_{mD} = 2\sqrt{k_n D I_{DQ}} \quad r_{oD} = (\lambda I_{DQ})^{-1}$$

C. 求 A_V 、 R_{in} 、 R_{out}

$$V_{gsL} = -V_O \quad V_{gsD} = V_i$$

$$i_{roD} = \frac{V_O}{r_{oD}} \quad i_{roL} = \frac{V_O}{r_{oL}}$$

$$g_{mL} V_{gsL} = 0$$

$$\text{A 點 KCL: } g_{mD} V_{gsD} + i_{roD} + i_{roL} = 0$$


$$\rightarrow \rightarrow g_{mD} V_i + \frac{V_O}{r_{oD}} + \frac{V_O}{r_{oL}} = 0$$

$$\rightarrow \rightarrow V_O \left(\frac{1}{r_{oD}} + \frac{1}{r_{oL}} \right) = -g_{mD} V_i$$



$$A_V = \frac{V_O}{V_i} = \frac{-g_{mD}}{\left(\frac{1}{r_{oD}} + \frac{1}{r_{oL}} \right)} = -g_{mD} (r_{oD} \parallel r_{oL})$$

$$R_{in} = r_{oD} \parallel r_{oL}$$

$$R_{out} = \infty$$

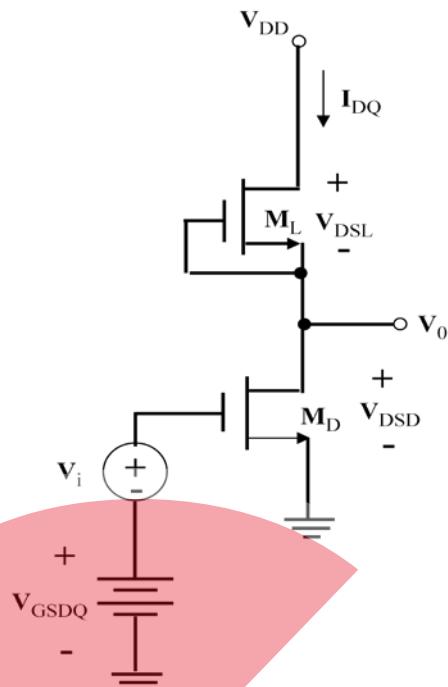

3. 具主動負載的 NMOS 放大器

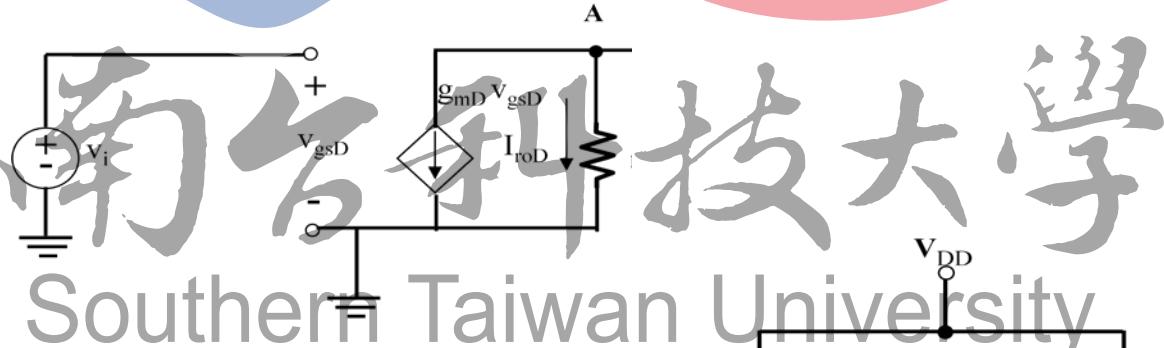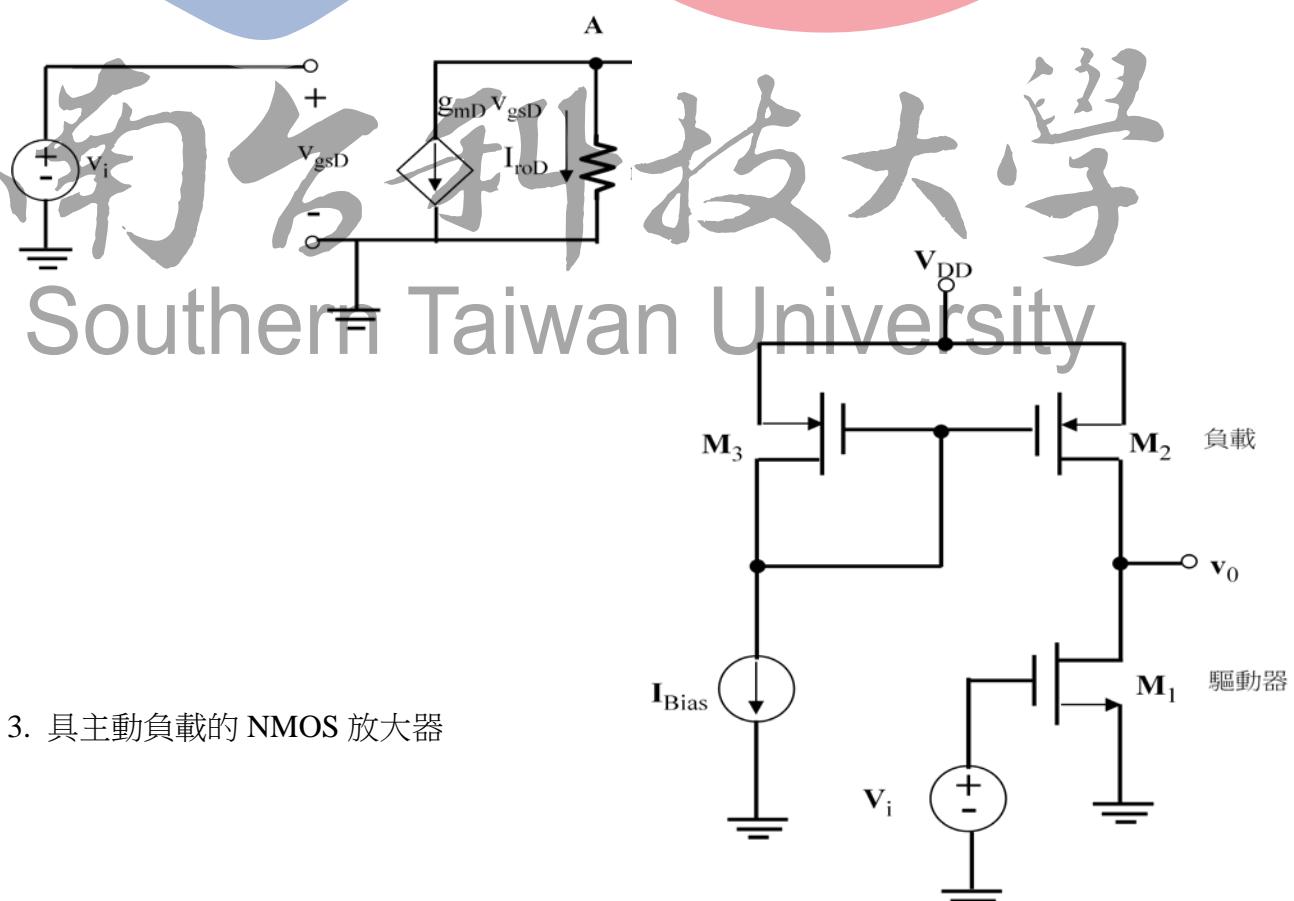

AC 分析

D. 畫出等效電路圖

E. 參數計算

$$g_{mL} = 2\sqrt{k_n L I_{DQ}} \quad r_{oL} = (\lambda I_{DQ})^{-1}$$

$$g_{mD} = 2\sqrt{k_n D I_{DQ}} \quad r_{oD} = (\lambda I_{DQ})^{-1}$$

F. 求 A_V 、 R_{in} 、 R_{out}

$$v_{sgL} = v_o \quad v_{gsD} = v_i$$

$$i_{roD} = \frac{v_o}{r_{oD}} \quad i_{roL} = \frac{v_o}{r_{oL}}$$

$$g_{mL} v_{sgL} = 0$$

$$\text{A 點 KCL: } g_{mD} v_{gsD} + i_{roD} + i_{roL} = 0$$

$$\rightarrow g_{mD} v_i + \frac{v_o}{r_{oD}} + \frac{v_o}{r_{oL}} = 0$$

$$\rightarrow v_o \left(\frac{1}{r_{oD}} + \frac{1}{r_{oL}} \right) = -g_{mD} v_i$$

$$A_V = \frac{v_o}{v_i} = \frac{-g_{mD}}{\left(\frac{1}{r_{oD}} + \frac{1}{r_{oL}} \right)} = -g_{mD} (r_{oD} \parallel r_{oL})$$

$$R_{in} = r_{oD} \parallel r_{oL}$$

$$R_{out} = \infty$$

