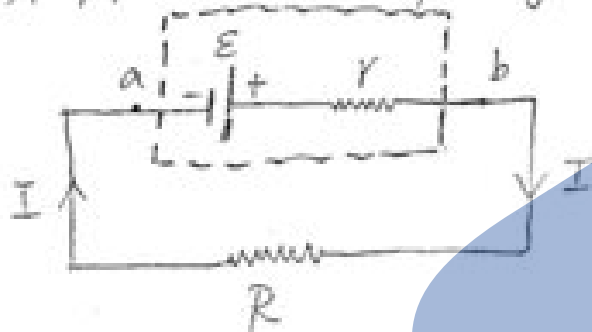


§18.1 Sources of emf




端電壓  $\Delta V = V_b - V_a$

$\Delta V = \text{電動勢 } \varepsilon - IR$

$\varepsilon = IR + IR$

$I = \frac{\varepsilon}{R + r}$

$I\varepsilon = I^2R + I^2r$

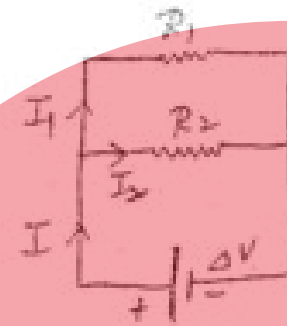

$I_1 = \frac{\Delta V}{R_1}$     $I_2 = \frac{\Delta V}{R_2}$

$I = \frac{\Delta V}{R_{eq}}$


$I = I_1 + I_2$

$\frac{\Delta V}{R_{eq}} = \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2}$

$\boxed{\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}}$

Example 18.2

18.2 Resistors in Series  
電阻 串聯

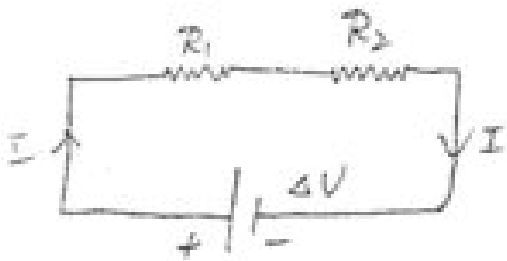

$\Delta V = IR_1 + IR_2 = I(R_1 + R_2)$

$\Delta V = I R_{eq}$

$\boxed{R_{eq} = R_1 + R_2}$

Example 18.1

Example 18.3

南方科技大學

Southern Taiwan University

# § 18.4 Kirchhoff's Rules and Complex DC Circuits


基爾荷夫定律

Kirchhoff's rules:

1. The sum of the currents entering any junction must equal the sum of the currents leaving that junction. (This rule is often referred to as the junction rule.)
2. The sum of the potential differences across all the elements around any closed-circuit loop must be zero. (This rule is usually called the loop rule.)

## Example 18.4

## § 18.5 RC Circuits

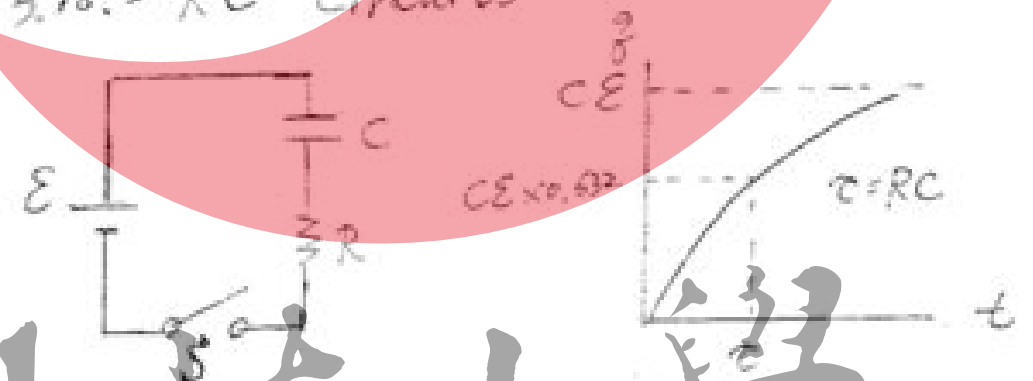


$$q = Q(1 - e^{-t/RC})$$

$$\Delta V = \frac{q}{C}$$


Time constant  $\tau = RC$

南方科技大學

Southern Taiwan University

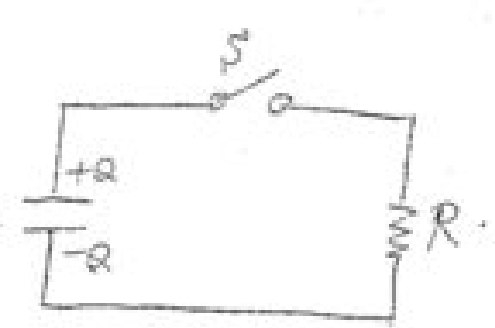

$$q = Q e^{-t/RC}$$

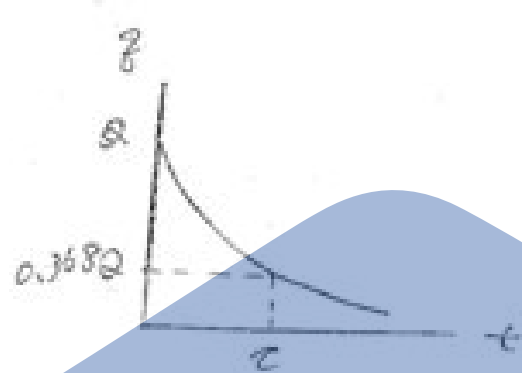

Example 18.5

南台科技大學

Southern Taiwan University