


## Chapter 6

# 基本雙極電晶體放大電路

### 6.2 雙極線性放大器

## 6.2 雙極線性放大器

### ◆ 小訊號混和 $\pi$ 模型的等效電路

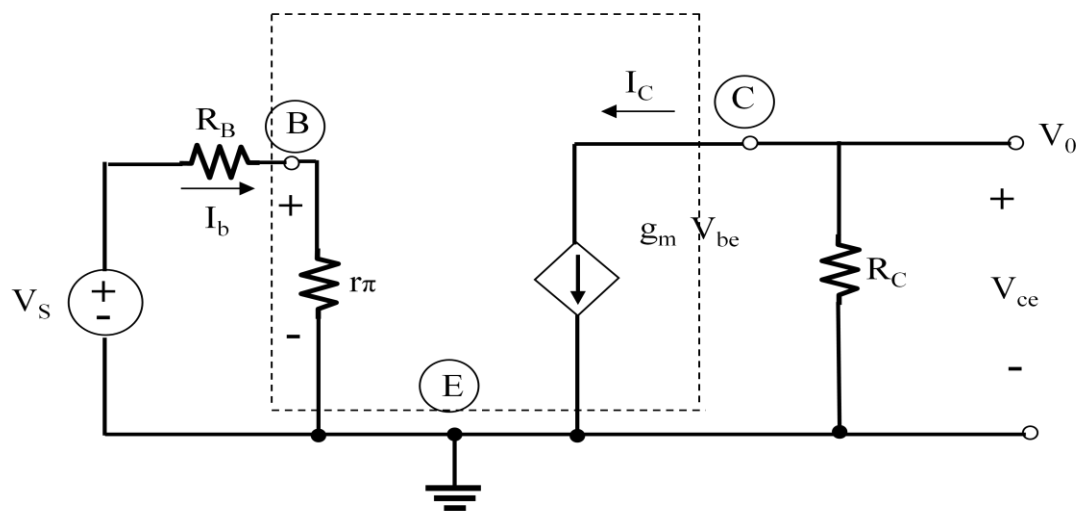

$$i_b = \frac{I_{BQ}}{V_T} v_{be}$$

$$v_{be} = \frac{V_T}{I_{BQ}} i_b$$

定義:  $\frac{v_{be}}{i_b} = r_{\pi}$  稱為擴散電阻 (Diffusion Resistance)

由上述兩式得  $r_{\pi} = \frac{V_T}{I_{BQ}}$

$$i_c = \left( \frac{\beta}{1 + \beta} \right) I_S e^{\frac{v_{be}}{V_T}} = \alpha I_S e^{\frac{v_{be}}{V_T}}$$

$$\frac{\partial i_c}{\partial v_{be}} = \left( \alpha I_S e^{\frac{v_{be}}{V_T}} \right) \frac{1}{V_T} = I_{CQ} \frac{1}{V_T}$$

此時  $\frac{\Delta i_c}{\Delta v_{be}} = I_{CQ} \frac{1}{V_T} = g_m v_{be}$


定義:  $g_m$  稱為轉導 (Transconductance)

$$i_c = g_m v_{be} = \beta i_b$$

$$g_m \left( \frac{v_{be}}{i_b} \right) = \beta$$

$$g_m r_{\pi} = \beta$$

◆ 含有厄利效應的混成  $\pi$  等效電路

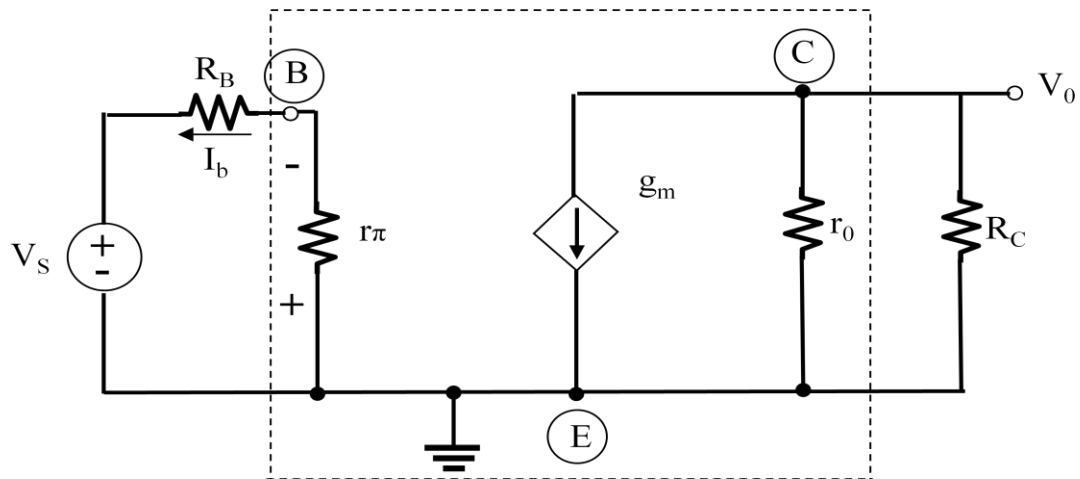

在之前章節討論過厄利效應，就是集極電流其實會隨著集極電壓而改變。

$$I_C = I_S e^{\frac{v_{be}}{V_T}} \left( 1 + \frac{V_{CE}}{V_A} \right) \text{ 其中 } V_A \text{ 為厄利電壓}$$

$$r_o = \frac{\partial V_{CE}}{\partial I_C}$$

$$\frac{1}{r_o} = \frac{\partial I_C}{\partial V_{CE}} = \frac{\partial}{\partial V_{CE}} \left\{ I_S e^{\frac{v_{be}}{V_T}} \left( 1 + \frac{V_{CE}}{V_A} \right) \right\}$$

$$\text{解出上式即可得 } r_o = \frac{V_A}{I_{CQ}}$$

將  $r_o = \frac{V_A}{I_{CQ}}$  定義為小訊號電晶體輸出電阻

(Small – Signal Transistor Output Resistance)